

# Application Note: Reference Design Explanation

---

# Table of Contents

- 1. Introduction..... 4
- 2. Reference Design Versions..... 5
  - 2.1 SX1261 PCB\_E406V03A..... 5
    - 2.1.1 E406V03A Schematic..... 5
    - 2.1.2 E406V03A PCB..... 7
  - 2.2 SX1262 PCB\_E428V03A..... 9
    - 2.2.1 E428V03A Schematic..... 9
    - 2.2.2 E428V03A PCB..... 10
  - 2.3 SX1262 PCB\_E449V01A..... 13
    - 2.3.1 E449V01A Schematic..... 13
    - 2.3.2 E449V01A PCB..... 14
- 3. Transmitter Impedance Matching and Filter Designs..... 17
  - 3.1 Impedance Matching Stage..... 17
    - 3.1.1 Load-Pull ..... 18
    - 3.1.2 Impedance Matching ..... 19
    - 3.1.3 Harmonic Filtering..... 20
- 4. Receiver Balun and Impedance Matching..... 21
- 5. Conclusion..... 22
- 6. Revision History..... 23
- 7. Glossary..... 24

---

## List of Figures

Figure 1: SX1261 Reference Design Schematic (PCB_E406V03A) .....	6
Figure 2: SX1261 Reference Design Layout – Top Layer (PCB_E406V03A) .....	7
Figure 3: SX1261 Reference Design Layout – Top Layer RF only (PCB_E406V03A).....	8
Figure 4: SX1261 Reference Design Layout – Bottom Layer (PCB_E406V03A) .....	8
Figure 5: SX1262 Reference Design Schematic (PCB_ E428V03A) .....	9
Figure 6: SX1262 Reference Design Layout – Top Layer (PCB_ E428V03A) .....	10
Figure 7: SX1262 Reference Design Layout – Layer 2 (PCB_ E428V03A).....	11
Figure 8: SX1262 Reference Design Layout – Layer 3 (PCB_ E428V03A).....	11
Figure 9: SX1262 Reference Design Layout – Bottom Layer (PCB_ E428V03A) .....	12
Figure 10: SX1262 Reference Design Schematic (PCB_ E449V01A) .....	13
Figure 11: SX1262 Reference Design Layout – Top Layer (PCB_ E449V01A).....	14
Figure 12: SX1262 Reference Design Layout – Layer 2 (PCB_ E449V01A) .....	15
Figure 13: SX1262 Reference Design Layout – Layer 3 (PCB_ E449V01A) .....	15
Figure 14: SX1262 Reference Design Layout – Bottom Layer (PCB_ E449V01A).....	16
Figure 15: SX1261 Transmitter and Receiver Matching/Filtering Topologies.....	17
Figure 16: Load-Pull Data of SX1261 at 915 MHz.....	18
Figure 17: Simulation of Transmitter Matching Network .....	19
Figure 18: SX1261 Source Pull Data at 915 MHz .....	21

---

# 1. Introduction

The purpose of this application note is to assist engineers with the selection of optimal reference design and understanding of the key components and design methodology deployed in each design of the SX1261 and SX1262.

It is recommended to read this application note in conjunction with the following documents which can be found on [www.semtech.com](http://www.semtech.com):

- Application Note AN1200.37 “Recommendations for Best Performance”
- SX1261/2 Datasheet

## 2. Reference Design Versions

There are currently three versions of SX1261/2 reference designs which cover the majority of the sub-GHz ISM frequency bands around the world. The reference designs are available upon request to your Semtech representative.

Table 1: SX1261/2 Reference Designs & Sub-GHz ISM Frequency Bands around the World

PCB #	Part	PCB Layer	Reference	Region	Band [MHz]
PCB_E406V03A	SX1261	2	XTAL	Europe	863 – 870
				Rest of Asia	923
				South Korea	920 - 923
PCB_E428V03A	SX1262	4	XTAL	USA, Canada	902 - 928
PCB_E449V01A	SX1262	4	TCXO	Australia	915 - 928
				India	865 - 867

### 2.1 SX1261 PCB\_E406V03A

The SX1261 reference design (E406V03A) is optimized to support all sub-GHz ISM frequency bands. It's designed to deliver +14 dBm of output power with only 25.5 mA of current consumption at 3.3V. It can even be programmed to deliver up to +15 dBm of output power for applications where antenna loss is expected. Each region has its dedicated bill of materials.

#### 2.1.1 E406V03A Schematic

The SX1261 E406V03A schematic is illustrated below in Figure 1. From the schematic, it can be observed that the transmit and receive paths are combined by a Peregrine PE4259 RF switch. The use of the RF switch facilitates the optimization of transmitter and receiver matching networks and filtering, which ultimately improves receive sensitivity and transmit output power and harmonic performance.

The power amplifier output stage (RFO) of the SX1261 is biased by an internal regulator output (VR\_PA) through an external pull-up inductor. In turn, the VR\_PA regulator is powered by either an internal LDO or a DC - DC converter through the VDD\_IN pin. The choice between using the internal LDO or the DC - DC converter ultimately comes down to the tradeoffs between PCB size, component cost, and power efficiency. On one hand the internal LDO offers the benefits of smaller size, and lower cost through the elimination of a large inductor between pins 7 and 9, but at the expense of power efficiency. On the other hand, the DC - DC converter offers higher power efficiency, but at the expense of size and cost. Output power varies with changing VR\_PA, but is kept relatively constant

over the entire main supply voltage of 1.8 to 3.7 V. The current consumption however changes inversely with main supply voltage.

Despite smaller size and lower cost, the default configuration of the SX1261 E406V03A reference design is powered by DC - DC. The benefit of lower power consumption, along with the deployment of thermal relief, enables the use of a low-cost crystal as reference instead of a TCXO.

To choose the LDO regulator, the inductor between pin VDD\_IN and pin VREG is replaced by a short and the inductor between VREG and DCC\_SW is removed.

 


Figure 1: SX1261 Reference Design Schematic (PCB\_E406V03A)

## 2.1.2 E406V03A PCB

This SX1261 reference design (PCB\_E406V03A) was designed on a low-cost, standard two-layer FR-4 substrate. The top layer houses all of the components and critical RF layout. The bottom layer serves as ground and control routing.

To mitigate the impact of reference frequency drift on receive performance due to high heat dissipation of the SX1261, extra precautions were taken to isolate the crystal from the rest of the PCB on all layers. As shown in Figures 2 and 3, a copper void around the reference was implemented on all layers.

 


Figure 2: SX1261 Reference Design Layout – Top Layer (PCB\_E406V03A)

 


Figure 3: SX1261 Reference Design Layout – Top Layer RF only (PCB\_E406V03A)

 


Figure 4: SX1261 Reference Design Layout – Bottom Layer (PCB\_E406V03A)

## 2.2 SX1262 PCB\_E428V03A

The SX1262 reference design (PCB\_E428V03A) is designed for regions that support higher output, while still tolerating the use of a crystal as clock reference thanks to the maximum packet duration of less than 400 milliseconds. The optimized bill of materials for the supported regions (USA and Canada) enable the reference design to deliver up to +22 dBm, while maintaining a current consumption of around 118 mA at 3.3 V.

### 2.2.1 E428V03A Schematic

The schematic as shown in Figure 5 is almost identical to the SX1261 two-layer reference design (PCB\_E406V03A). The key difference is that VDD\_IN, source of the internal regulator VR\_PA, is powered directly from the battery VBAT pin instead of VREG. This is still a DC - DC supplied configuration, where the DC - DC is used for the chip core only.

 


Figure 5: SX1262 Reference Design Schematic (PCB\_E428V03A)

## 2.2.2 E428V03A PCB

The key difference between this SX1262 PCB design versus the SX1261 two-layer design is that the former deploys a four-layer FR-4 substrate instead of a two-layer substrate. The primary reasons are that it is intended to deliver output powers of up to +22 dBm, thermal dissipation is more critical, and it's not as cost-sensitive as the other applications.

In this design, the top layer remains dedicated to all components and critical RF routing. Layer 2 serves as reference ground for all RF circuitries, layer 3 is used for control routing, and layer 4 is solid ground.

In a similar way to the SX1261 two-layer design, a copper void was created around the crystal reference, on all layers, to mitigate the thermal effects on frequency drift.

 


Figure 6: SX1262 Reference Design Layout – Top Layer (PCB\_E428V03A)

 


Figure 7: SX1262 Reference Design Layout – Layer 2 (PCB\_ E428V03A)

 


Figure 8: SX1262 Reference Design Layout – Layer 3 (PCB\_ E428V03A)

 


Figure 9: SX1262 Reference Design Layout – Bottom Layer (PCB\_ E428V03A)

## 2.3 SX1262 PCB\_E449V01A

The SX1262 reference design (PCB\_E449V01A) is designed for regions that support high output and maximum packet durations beyond 400 milliseconds; thus requiring the use of a four-layer board PCB and TCXO as clock reference. The optimized bill of materials for the supported regions (Australia and India) enable the reference design to deliver up to +22 dBm, while maintaining currently consumption of around 118 mA at 3.3V.

### 2.3.1 E449V01A Schematic

The schematic as shown in Figure 10 is almost identical to the SX1262 four-layer reference design (PCB\_E428V03A). The key difference is in the use of a TCXO as clock reference instead of a crystal. It was experimentally proven that two- and four-layer boards equipped with crystal and thermal insulation similar to PCB\_E406V03A and PCB\_E428V03A were still exceeding the tolerable frequency drifts in regions where maximum packet duration could be as high as 2.8 seconds.

 


Figure 10: SX1262 Reference Design Schematic (PCB\_E449V01A)



 


Figure 12: SX1262 Reference Design Layout – Layer 2 (PCB\_ E449V01A)

 


Figure 13: SX1262 Reference Design Layout – Layer 3 (PCB\_ E449V01A)

 


Figure 14: SX1262 Reference Design Layout – Bottom Layer (PCB\_E449V01A)

# 3. Transmitter Impedance Matching and Filter Designs

The primary objective of impedance matching and harmonic filtering is to achieve the maximum power transfer from the PA output to the antenna, while consuming the least amount of power and emitting the lowest level emissions in order to meet the regulatory requirements. Here we take as example the SX1261 at 915 MHz. The methodology used is applicable to both SX1261 and SX1262, at all frequencies.

The transmitter impedance matching/filtering can be split into 3 sections: the impedance matching stage, the second harmonic filtering stage, and the higher order harmonic filtering stage.

As shown in Figure 15, the chosen matching topology consists of L3 and C5, the second order harmonic filter consists of L3 and C4, and the higher order harmonic filter consisting of C5, L4 and C7. C6 serves as a DC block to protect the input of the RF switch. The expected input impedance to the RF switch is 50 ohms. The network at the output of the RF switch is primarily there to offer optimal matching to the antenna, but additional filtering can also be achieved through such network.

 


Figure 15: SX1261 Transmitter and Receiver Matching/Filtering Topologies

## 3.1 Impedance Matching Stage

In order to maximize power transfer and minimize power consumption, an optimal impedance  $Z_{opt}$  must be presented to the output of the power amplifier. Although L3 and C5 have been identified as the primary impedance matching components, the remaining filtering components C4/L3 and C6/L4/C7 will also contribute to the effective load impedance seen by the power amplifier.

Therefore, it's important to include all three stages of impedance transformation and filtering when designing the network which represents the  $Z_{opt}$ . The load-pull data and impedance matching components shown below may not be the most up-to-date. Contact your Semtech representative for the latest information per reference design.

## 3.1.1 Load-Pull

To obtain  $Z_{opt}$ , a load-pull analysis is typically conducted using an impedance tuner and network analyzer, referenced to the PA output pad (RFO) of SX1261/2. During this process, the load presented to the PA output is swept in magnitude and phase while recording the output power and current consumption. The results are then plotted on a Smith chart in the Figure 16, the highest output power of 14.6 dBm at 915 MHz was identified to be at an impedance of  $11.7 + j4.8$  ohms, while  $13.5 + j7.6$  ohms offers lower output power but with higher efficiency.

**Note:** the configuration explained here is meant to obtain an optimal +14 dBm power output at the end of the chain consisting of matching, filtering and RF switch, anticipating losses due to these last stages.

SX1261V2A Load Pull - 915 MHz - paDcTrim = 4  
Pmax = 14.6 dBm, IDDTX = 53.3 mA, Zopt = 11.7 + j4.8 Ohm  
Pout = 14.5 dBm, IDDTX = 47.8 mA, Zopt = 13.5 + j7.6 Ohm  
Pout > 14.5 dBm (all points)

 


Figure 16: Load-Pull Data of SX1261 at 915 MHz

To ensure that the peak power impedance point has been identified, data at a power level roughly lower than 1 dB were also plotted. If this is implemented correctly, the peak power impedance on

the graphic would be somewhere near the center of all the points. With this information, the designer can then choose the appropriate Zopt based on desired output power and power consumption.

### 3.1.2 Impedance Matching

Once the Zopt and the impedance matching have been identified, the next steps would be to come up with a practical matching and filtering topology, and simulate the theoretical values by using tools such as Agilent ADS and Ansoft Designer.

The goal of the impedance matching stage is to present the optimum load impedance to the SX1261/SX1262 PA when matched to 50 ohms. In order to minimize the number of components for the matching network, this will be done using L3 and C5 of the TX stage.

 


Figure 17: Simulation of Transmitter Matching Network

In reality, it's often necessary to fine-tune the simulated values to account to PCB parasitic and practical component values.

---

## 3.1.3 Harmonic Filtering

Harmonic filtering is implemented in two stages: the second harmonic notch filter and the higher order harmonic low-pass filter.

The notch filter is implemented by replacing the original L3 with a parallel LC filter. As a general rule of thumb, the new inductor value is chosen to be 3/4 of the original L3, and C4 is calculated to resonate out the second harmonic of the carrier frequency.

The higher order harmonic filter is a 50-ohm to 50-ohm pi filter, realized on C5, L4, C6, and C7. C5 is therefore used for both the impedance matching and the harmonic filtering, and its value will be the sum of the two values obtained separately.

Again, it's often necessary to fine-tune the simulated values to account for PCB parasitic and practical component values.

The last step would be to add the PE4259 RF switch and redo the measurements. Additional filtering and impedance matching to any non-50-ohm antenna can be accommodated by utilizing C8, C9, L5, and C10.

## 4. Receiver Balun and Impedance Matching

The low-noise amplifier (LNA) of the SX1261/2 is designed with differential inputs for the benefit of common mode rejection and immunity against noise and interferers.

The LC network in front of the differential inputs serves both functions of a balun to convert the single-ended to differential signals and impedance transformation. As shown in Figure 15, this network consists of two capacitors (C11, C12) and one inductor (L6). C13 is an optional element which could be used to provide additional rejection against undesired interferers.

In a similar way to the transmitter, the primary objective of impedance matching on the receiver front-end is to transform the ideally 50-ohm impedance at the RF switch output to the desired optimal impedance ( $Z_{opt}$ ) of the SX1261/2 differential LNA inputs.

The steps to identify the optimal source impedance and simulating/implementing the matching network are similar to the ones deployed on the transmitter. A source pull was first conducted to identify the optimal impedance which delivers the lowest noise figure, as shown in Figure 18. In the case of SX1261 at 915 MHz, the optimal differential source impedance is  $74 + j134$ .

 


Figure 18: SX1261 Source Pull Data at 915 MHz

---

## 5. Conclusion

In summary, this application note clarified some of the key differences between the available reference designs, and the major advantages and disadvantages between 2-layer versus 4-layer substrates, LDO regulator versus DC - DC converter, and XTAL versus TCXO. It also explained the methodology on how the transmit and receive performances were optimized.

---

# 6. Revision History

Version	Date	Modifications
1.0	December 2017	First Release
1.1	May 2018	Update of PCB part numbers and schematics

---

## 7. Glossary

DC-DC	Direct Current to Direct Current (power conversion)
ISM	Industrial, Scientific and Medical applications
LDO	Low Dropout
LNA	Low-Noise Amplifier
LoRa®	Long Range modulation technique
LoRaWAN™	LoRa® low power Wide Area Network protocol
PA	Power Amplifier
PCB	Printed Circuit Board
RF	Radio-Frequency
RFO	Radio Frequency Output
RX	Receiver
SW	Software
TCXO	Temperature-Compensated Crystal Oscillator
TX	Transmitter
VDD	Voltage Drain Drain
VREG	Voltage Regulator
XTAL	Crystal



---

## Important Notice

Information relating to this product and the application or design described herein is believed to be reliable, however such information is provided as a guide only and Semtech assumes no liability for any errors in this document, or for the application or design described herein. Semtech reserves the right to make changes to the product or this document at any time without notice. Buyers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. Semtech warrants performance of its products to the specifications applicable at the time of sale, and all sales are made in accordance with Semtech's standard terms and conditions of sale.

SEMTECH PRODUCTS ARE NOT DESIGNED, INTENDED, AUTHORIZED OR WARRANTED TO BE SUITABLE FOR USE IN LIFE-SUPPORT APPLICATIONS, DEVICES OR SYSTEMS, OR IN NUCLEAR APPLICATIONS IN WHICH THE FAILURE COULD BE REASONABLY EXPECTED TO RESULT IN PERSONAL INJURY, LOSS OF LIFE OR SEVERE PROPERTY OR ENVIRONMENTAL DAMAGE. INCLUSION OF SEMTECH PRODUCTS IN SUCH APPLICATIONS IS UNDERSTOOD TO BE UNDERTAKEN SOLELY AT THE CUSTOMER'S OWN RISK. Should a customer purchase or use Semtech products for any such unauthorized application, the customer shall indemnify and hold Semtech and its officers, employees, subsidiaries, affiliates, and distributors harmless against all claims, costs damages and attorney fees which could arise.

The Semtech name and logo are registered trademarks of the Semtech Corporation. The LoRa® Mark is a registered trademark of the Semtech Corporation. All other trademarks and trade names mentioned may be marks and names of Semtech or their respective companies. Semtech reserves the right to make changes to, or discontinue any products described in this document without further notice. Semtech makes no warranty, representation or guarantee, express or implied, regarding the suitability of its products for any particular purpose. All rights reserved.

© Semtech 2018

---

## Contact Information

Semtech Corporation  
Wireless & Sensing Products  
200 Flynn Road, Camarillo, CA 93012  
E-mail: [sales@semtech.com](mailto:sales@semtech.com)  
Phone: (805) 498-2111, Fax: (805) 498-3804  
[www.semtech.com](http://www.semtech.com)